
ECE | VLSI

EMERGENCY PANIC ALARM BOARD

KiCad PCB Design Project

Lakshay Yadav

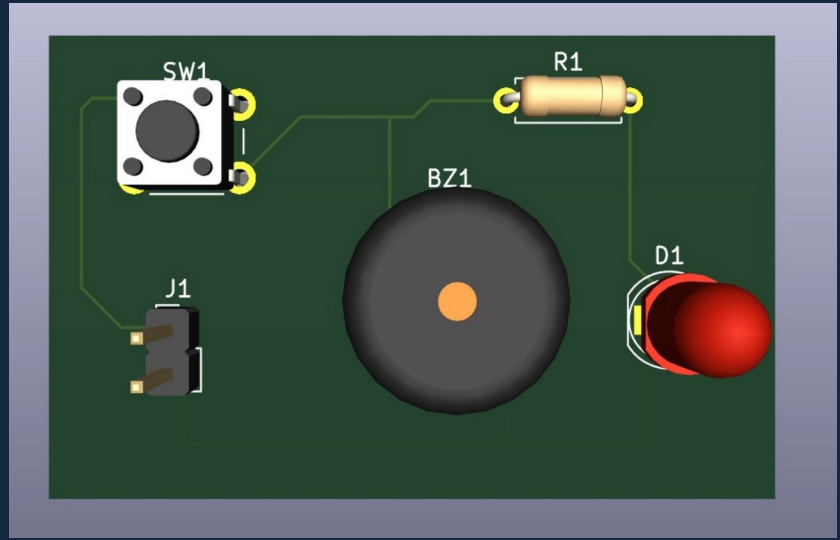Schematic • PCB Layout • 3D View • Gerber Output



A simple 5V panic-alert circuit

Pressing the push button activates the buzzer and warning LED.

5V INPUT
Power connector

›

PUSH
Momentary switch

›


ALERT
Buzzer + LED

Bill of Materials

J1	2-pin 5V power connector	1
SW1	Normally-open push button	1
BZ1	5V active buzzer	1
D1	Red LED	1
R1	330 Ω resistor	1


Schematic diagram

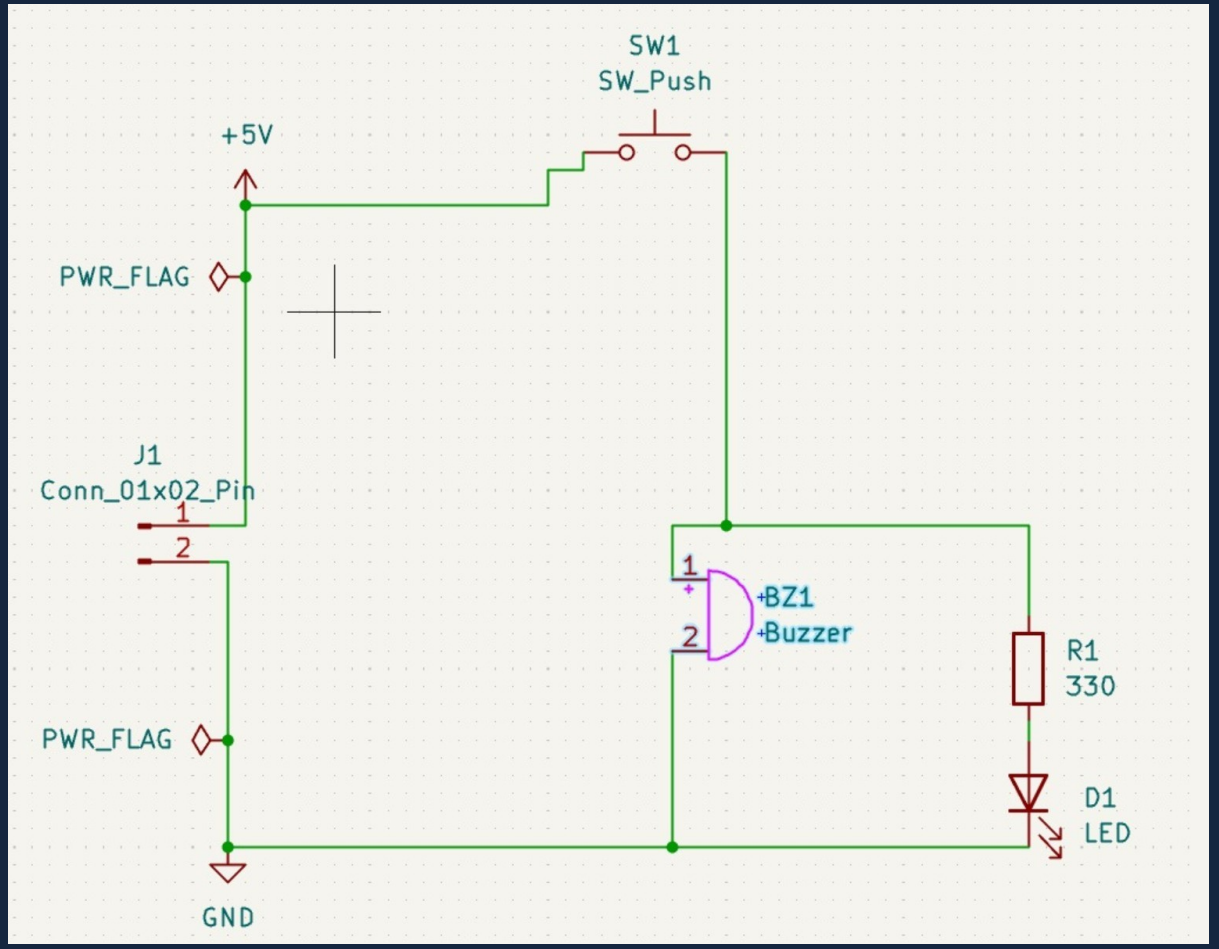Component symbols and electrical connections




Footprints after routing

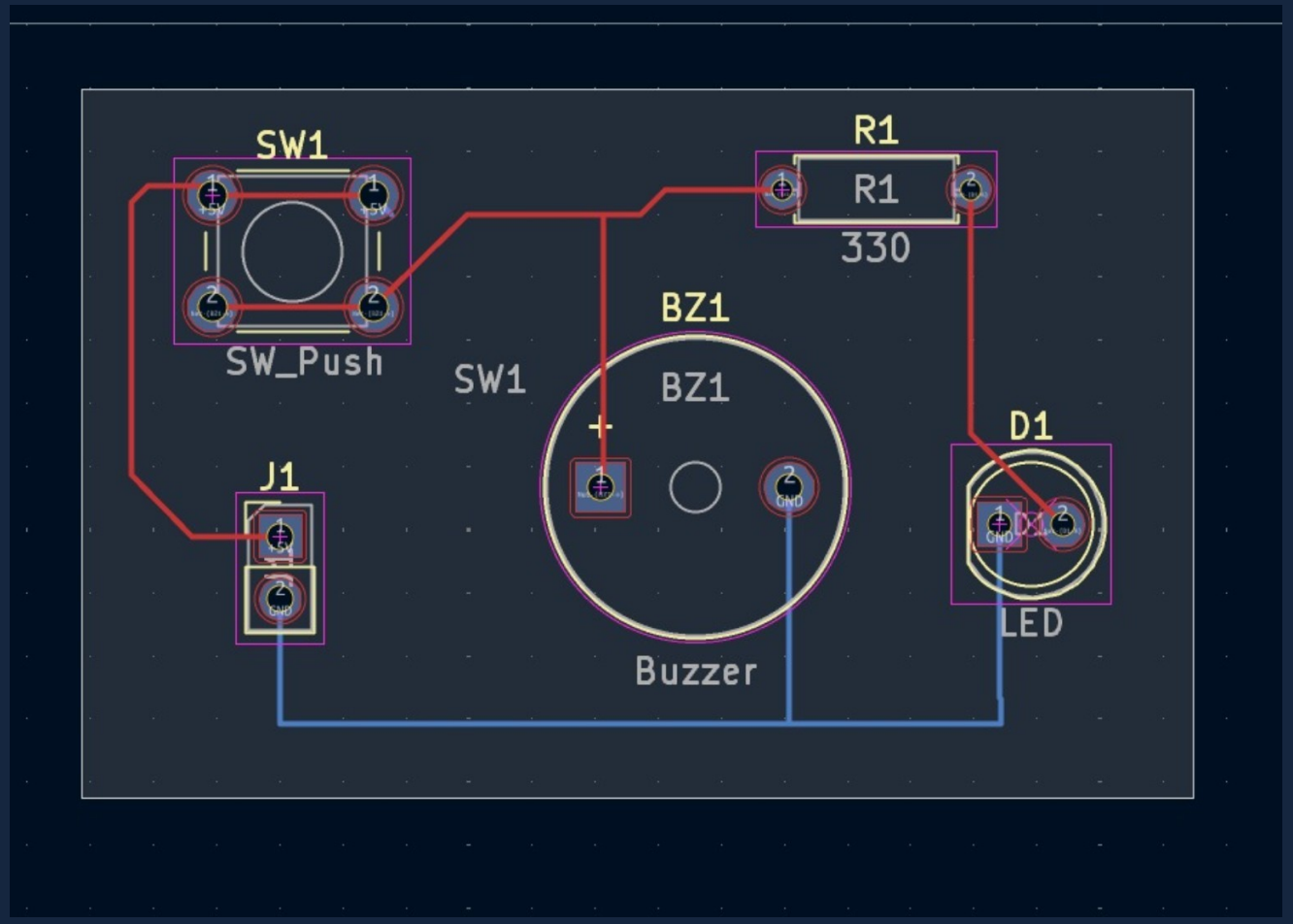All copper tracks routed • 0 unrouted connections




3D PCB view

Component placement and board appearance

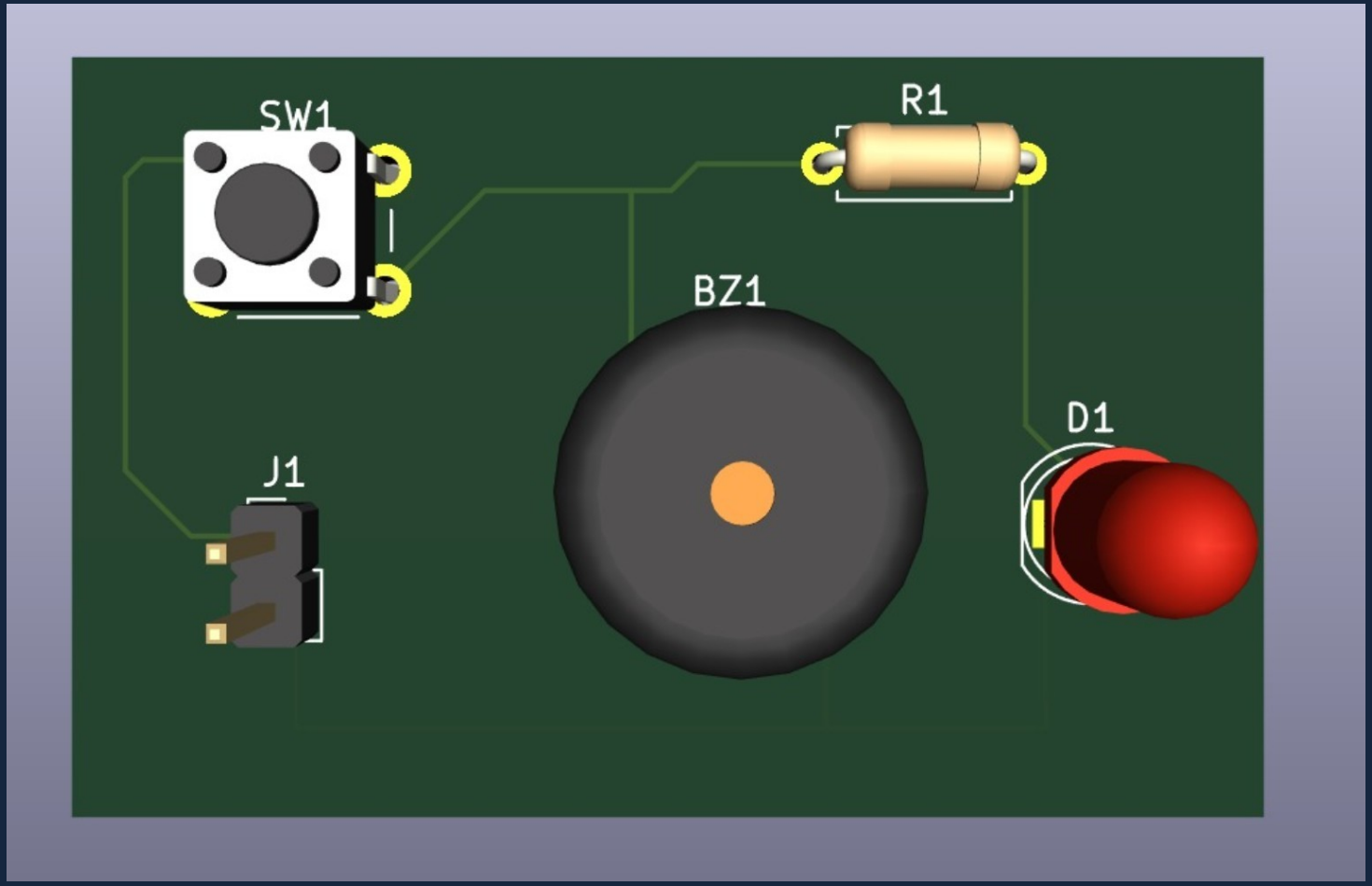

Gerber & drill output

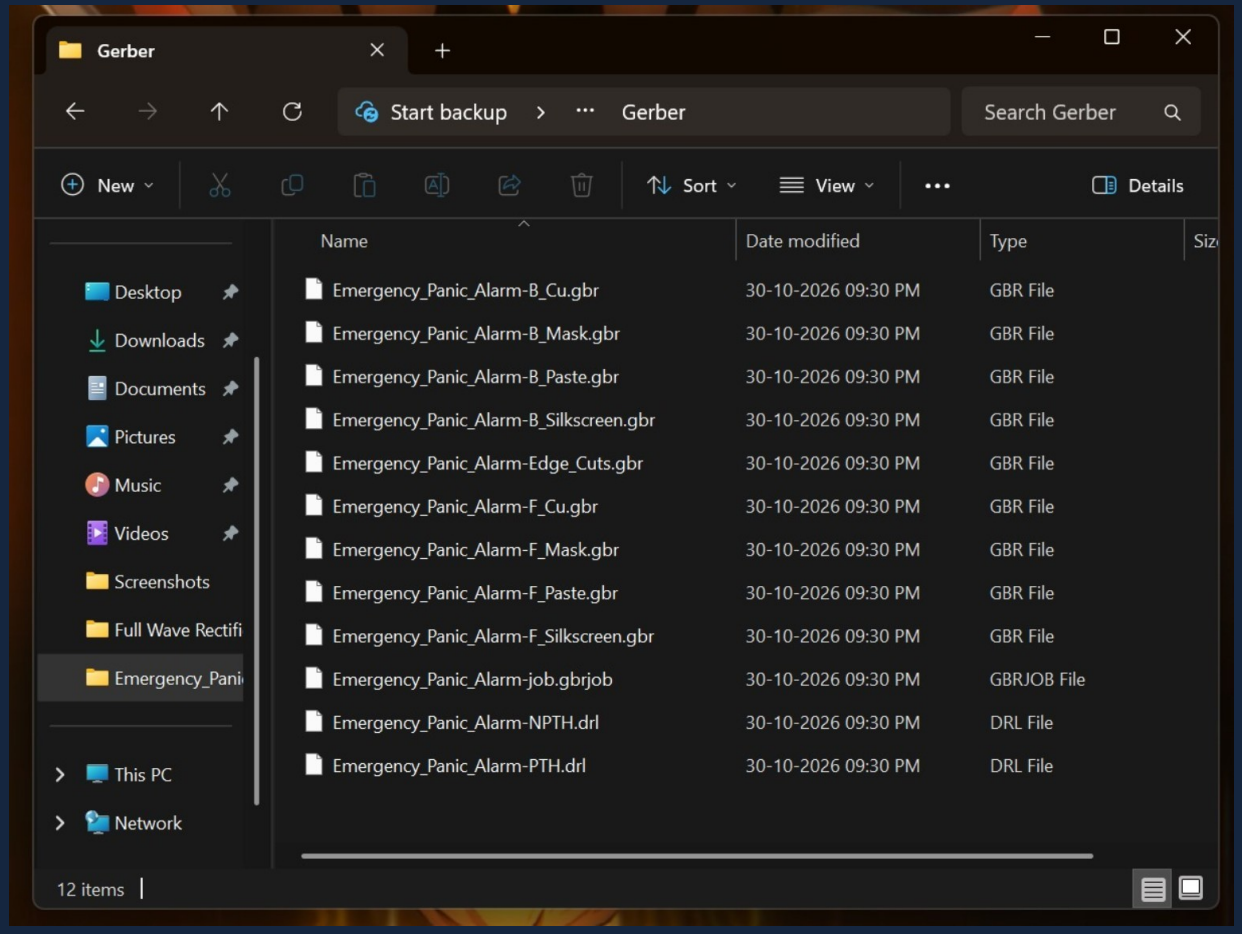Generated fabrication layers and drill files



Included layers

- F.Cu / B.Cu
- Solder mask
- Silkscreen
- Edge.Cuts
- PTH & NPTH drills

PROJECT COMPLETE

Emergency Panic Alarm Board

Designed in KiCad



Lakshay Yadav | ECE VLSI